



UNIVERSITY OF COLOMBO, SRI LANKA

FACULTY OF TECHNOLOGY

LEVEL I EXAMINATION IN TECHNOLOGY - SEMESTER II- 2022

IA 1301 – ANALOG AND DIGITAL ELECTRONICS I

Two (02) hours

Answer only 4 questions.

Electronic calculators are allowed.

No. of pages: 13

Important Instructions to Candidates

- If a page or part of this question paper is not printed, please inform the supervisor immediately.
- Enter your index number on all pages of the answer script.
- Write the answers to the questions in the space provided in the question paper.
- Electronic devices capable of storing and retrieving text, including electronic dictionaries and mobile phones are not allowed.
- If you have any doubt about the interpretation of the wording of a question, make your own assumption, but clearly state it in the script.

Index No:

Q	M
1	
2	
3	
4	
5	
Total	

01. You are asked to design a 1 kW single-phase full bridge diode rectifier to drive a DC motor. The DC motor rated voltage and current are 120 V and 8 A respectively.

(a). Draw the circuit diagram for the rectifier without the smoothing capacitor.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(3 marks)

(b). Calculate the required AC voltage (r.m.s) input to the rectifier.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(8 marks)

(c). Calculate the turns ratio of the required transformer if the supply voltage is 230 V (AC r.m.s).

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(3 marks)

- (d). Explain a method to vary the rectifier voltage output continuously.

[illegible]

(3 marks)

- (e). Assume that now a smoothing capacitor is connected to the output of the rectifier. Draw the rectifier input current waveform.

Hint: The output current waveform of the DC motor is purely DC.

[illegible]

(4 marks)

- (f). Briefly explain a method to obtain DC voltages in two polarities (positive and negative). Draw relevant circuit diagrams.

This image shows a full page of white paper with horizontal dashed lines, typical of primary school handwriting practice paper. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

(4 marks)

02. You are asked to design an inverting OP-AMP with a gain of 1000.

- (a). Draw the amplifier circuit and derive an equation for the output gain. Provide suitable values for the circuit elements.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(5 marks)

- (b). If the open loop gain of the OP-AMP IC is 100 000. Calculate the actual gain that is provided by the amplifier.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

(c). Draw the closed loop system diagram for the OP-AMP amplifier circuits.

[illegible]

(d). Show that for the inverting OP-AMP, $\frac{\text{Feedback resistance}}{\text{Input resistance}} \cong \frac{1}{\text{Feedback gain}}$

[illegible]

Page 5 of 13

03. Consider the transistor amplifier circuit shown in Figure 3.1.

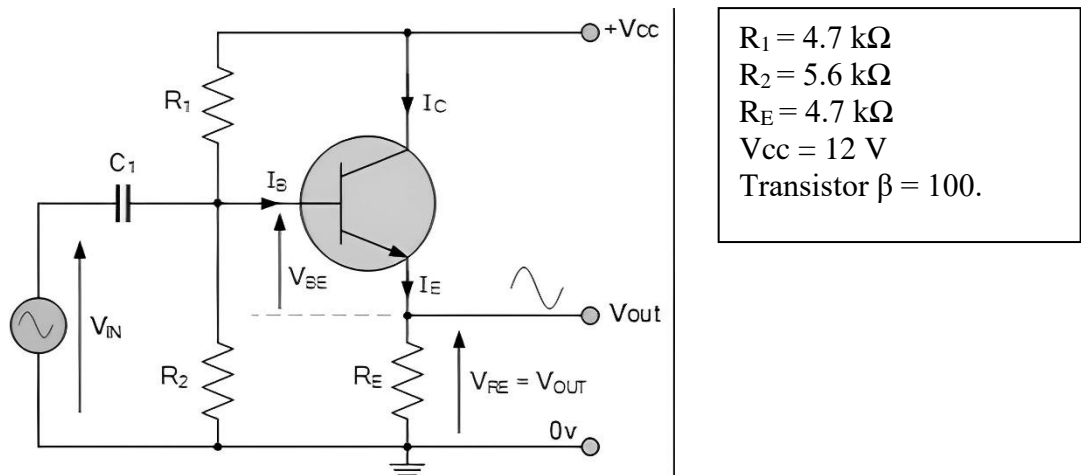


Figure 3.1 Transistor amplifier circuit

- (a). State the transistor amplifier configuration.

.....

(2 marks)

- (b). Calculate the base biasing voltage V_B .

.....

(3 marks)

- (c). Calculate the Emitter biasing voltage V_E and V_{CE} .

.....

(5 marks)

(d). Calculate the Emitter current I_E .

[illegible]

(3 marks)

(e). Draw $I_{C(SAT)}$ Vs. V_{CE} graph.

[illegible]

(5 marks)

(f). The output voltage is given by the following equation where the internal emitter resistance

$$r_e' \approx \frac{25 \text{ mV}}{I_E}.$$

$$V_{out} = \frac{V_{in} \times R_E}{r'_e + R_E}$$

Calculate the voltage gain of the amplifier.

[illegible]

(4 marks)

(g). What is the current gain of the amplifier?

.....

(3 marks)

04. a). A combinational logic circuit has three inputs (A , B and C) and two outputs (P and Q). The logic expression for P is given by,

$$P = A + \bar{A}\bar{B} + ABC$$

(i). Convert the logic expression for P into **standard** Sum of Products (SOP) form.

(4 marks)

.....

(ii). Hence fill the column corresponding to P in Table 4.1.

(2 marks)

Table 4.1

A	B	C	P	Q
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		1
1	0	0		1
1	0	1		1
1	1	0		0
1	1	1		0

- (iii). Obtain the **standard** Product of Sums (POS) expression for Q (in Table 4.1). (4 marks)

.....

.....

.....

.....

.....

- (iv). Obtain the most simplified SOP expression for Q . (4 marks)

.....

.....

.....

.....

.....

.....

.....

.....

.....

- (v). Construct the logic circuit for Q using two-input NAND gates. (4 marks)

- b). An indicator light has to be turned on in a vehicle dashboard when the driver or/and the passenger in the front seat have not fastened the seatbelts when the engine is on.

The indicator light is turned on when the output signal IND is 1.

The signal ENG becomes 1 when the engine is on. The signals from the pressure sensors in the driver seat and the passenger seat (D_seat and P_seat respectively) become 1 when

the seats are occupied. *D_belt* and *P_belt* signals from the seat belt buckles of the driver and the passenger seats become 1 when the belts are fastened.

Design the logic circuit for the above system.

Note: Constructing the truth table is not mandatory

(7 marks)

- 05.** a). What is the main difference between a latch and a flip-flop? (2 marks)

.....

.....

.....

.....

.....

- b). Construct a JK flip-flop by modifying a 'NAND gate based SR latch with an enable input'. Inputs and outputs must be labelled.

(5 marks)

- c). Show that a T flip-flop can be constructed using a JK flip flop (use the block diagram of JK flip flop).

(3 marks)

- d) (i). Consider Figure 5.1 and fill Table 5.1. (8 marks)

 


Figure 5.1

Table 5.1

A	B	Q_n	Q'_n	Q_{n+1}	Q'_{n+1}
1	0	0	1		
1	0	1	0		
0	1	0	1		
0	1	1	0		
1	1	0	1		
1	1	1	0		
0	0	0	1		
0	0	1	0		

- (ii). Hence identify the sequential logic device in Figure 5.1. (3 marks)

.....

- e). Consider the circuit in Figure 5.2 and complete the timing diagram in Figure 5.3. (4 marks)

 


Figure 5.2

 


Figure 5.3
